



34th International Symposium on Superconductivity (ISS 2021)  
ED5-1-INV

# Recent Progress in **A**diabatic **Q**uantum-**F**lux-**P**arametron Logic

N. Takeuchi<sup>1,2</sup>, C. L. Ayala<sup>2</sup>, C. Olivia<sup>3</sup>, N. Yoshikawa<sup>2</sup>

<sup>1</sup>Nat'l Inst. of Advanced Industrial Sci. & Tech. (AIST)

<sup>2</sup>Yokohama National University

<sup>3</sup>Tokyo City University

# Outline

2

- **Introduction to AQFP logic**
  - Adiabatic switching
  - Design methodology
  
- **Recent progress in AQFP logic**
  - Microprocessor
  - Single-photon image sensor
  - Stochastic electronics


# Outline

3

- **Introduction to AQFP logic**
  - Adiabatic switching
  - Design methodology
  
- **Recent progress in AQFP logic**
  - Microprocessor
  - Single-photon image sensor
  - Stochastic electronics

# Background


## Facebook data center in Sweden

 

- Performance: 27–51 PFLOPS
- Power: 84 MW avg (120 MW max)
- cf. Amagase dam: 92 MW (#4 in Kyoto)

D. S. Holmes, ISS 2013.

## Energy forecast

 

N. Jones, Nature **561**, 163 (2018).

- Rising power demand for ICT due to IoT, AI, Society 5.0, etc.
- Expected to reach 20.9% of global total power by 2030
- Extremely low-power computing systems required for future ICT

# Adiabatic quantum-flux-parametron (AQFP)

5

## Operating principle



- Powered by the ac excitation current  $I_x$
- $J_1$  and  $J_2$  generate the signal current  $I_s$ .
- Underdamped high- $J_c$  junctions used for low-energy op.

## Advantages

- ✓ Low energy dissipation
  - Zero static power
  - Adiabatic switching ( $\sim 10^{-21}$  J)
- ✓ High sensitivity (GZ  $< \sim 1$   $\mu$ A)
- ✓ Low-current drive ( $\sim$  mA)


Original QFP: M. Hosoya et al., IEEE TAS. **1** (1991).  
AQFP: N. Takeuchi et al., Supercond. Sci. Tech. **26** (2013).

## Basic gate

 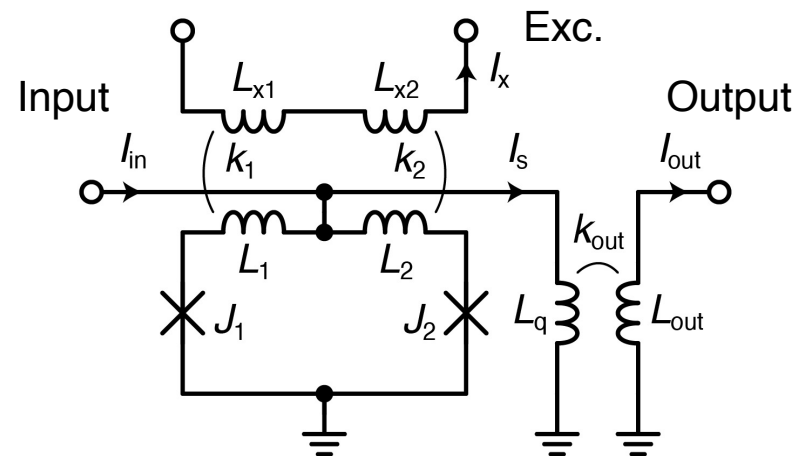


# Non-adiabatic vs. adiabatic switching

6

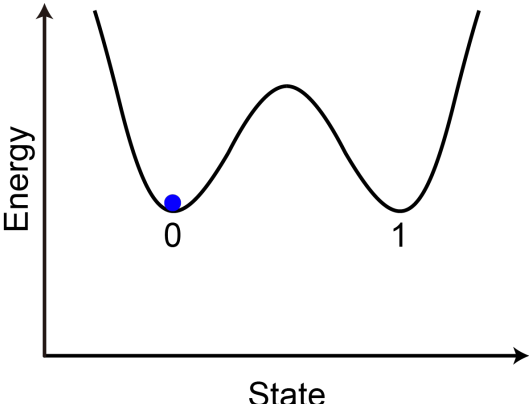Non-adiabatic switching	
Logic	CMOS, RSFQ etc.
Potential change while logic state switches	
Reversible?	
Work by a power supply	
Energy dissipation	



R. W. Keyes, Proc. IEEE **69** (1981).  
V. V. Zhirnov et al., Proc. IEEE **9** (2003).

# Non-adiabatic vs. adiabatic switching

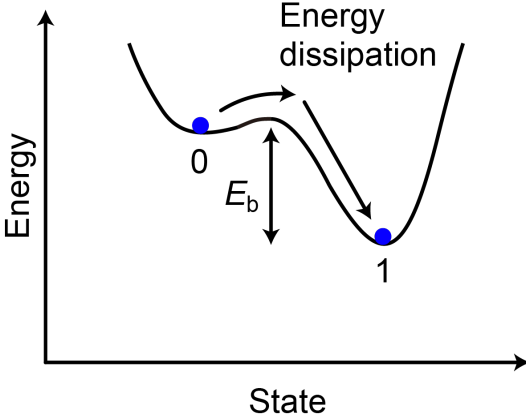Non-adiabatic switching	
Logic	CMOS, RSFQ etc.
Potential change while logic state switches	
Reversible?	No
Work by a power supply	Totally dissipated
Energy dissipation	$= E_b (\gg k_B T)$

R. W. Keyes, Proc. IEEE **69** (1981).  
 V. V. Zhirnov et al., Proc. IEEE **9** (2003).



# Non-adiabatic vs. adiabatic switching

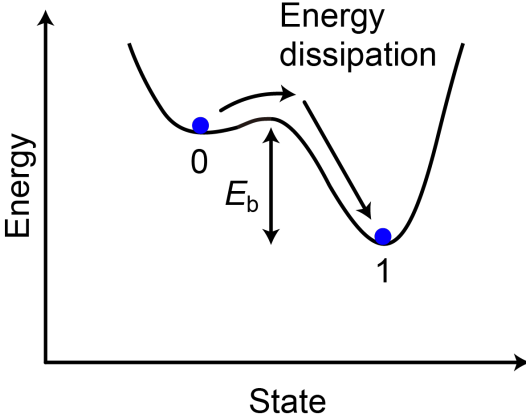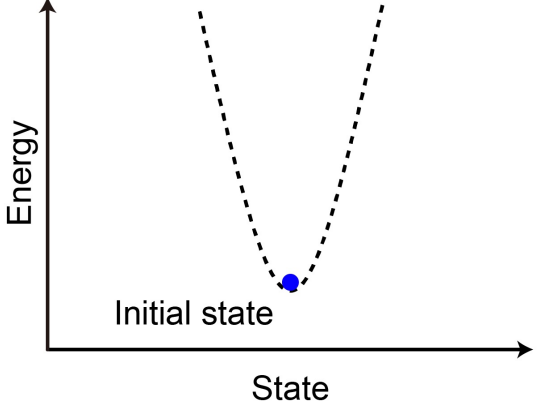	Non-adiabatic switching	Adiabatic switching
Logic	CMOS, RSFQ etc.	AQFP, nSQUID, PQ etc.
Potential change while logic state switches	 <p>Energy</p> <p>State</p> <p>Energy dissipation</p> <p>0</p> <p><math>E_b</math></p> <p>1</p>	 <p>Energy</p> <p>State</p> <p>Initial state</p>
Reversible?	No	
Work by a power supply	Totally dissipated	
Energy dissipation	$= E_b (\gg k_B T)$	

R. W. Keyes et al., IBM J. Res. Dev. **14** (1970).  
 K. Likharev, IEEE Trans. Magn. **13** (1977).




# Non-adiabatic vs. adiabatic switching

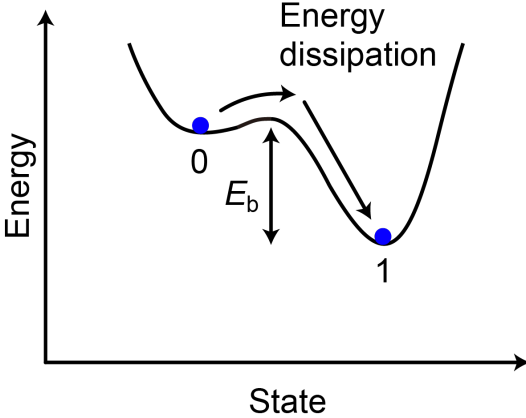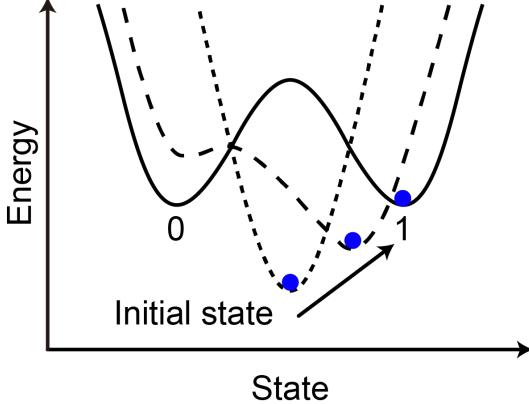	Non-adiabatic switching	Adiabatic switching
Logic	CMOS, RSFQ etc.	AQFP, nSQUID, PQ etc.
Potential change while logic state switches		
Reversible?	No	Yes
Work by a power supply	Totally dissipated	Not dissipated @ quasi-static
Energy dissipation	$= E_b (\gg k_B T)$	$\ll E_b$

R. W. Keyes et al., IBM J. Res. Dev. **14** (1970).  
 K. Likharev, IEEE Trans. Magn. **13** (1977).

# Switching energy of an AQFP gate

## Numerical simulation

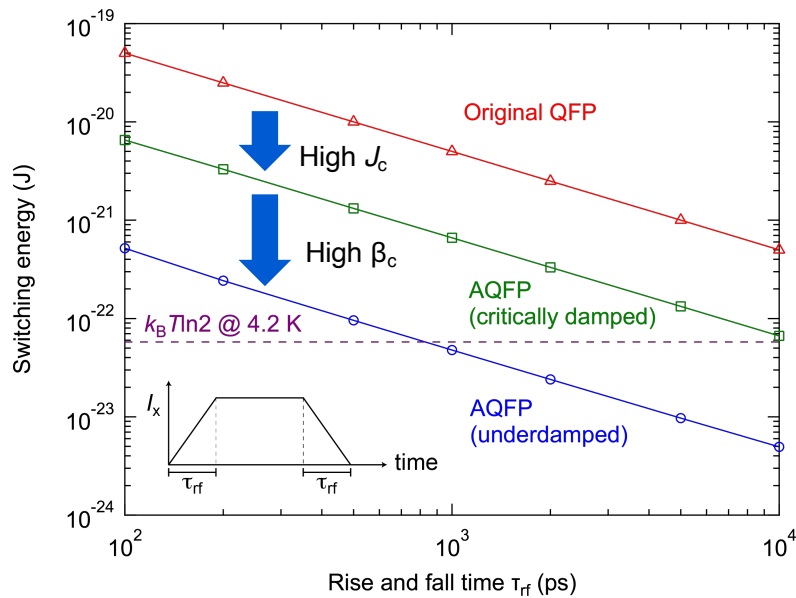

N. Takeuchi et al., Phys. Rev. Appl. 4 (2015).

## Analytical estimation

$$E_{SW} \propto I_c \Phi_0 \frac{(\sqrt{\beta_c J_c})^{-1}}{\tau_{rf}}$$

Annotations for the equation:
 

- 'Characteristic time' points to  $\tau_{rf}$ .
- 'Energy scale' points to  $I_c \Phi_0$ .
- 'Duration time' points to  $\tau_{rf}$ .
- ' $(\sqrt{\beta_c J_c})^{-1}$ ' is annotated with a blue arrow pointing to the term.

$\tau_{rf}$ : Rise time of excitation current

$\beta_c$ : McCumber parameter


$I_c$ : Critical current of junctions

$J_c$ : Critical current density

Switching energy can fall below  $k_B T \ln 2$  by lowering frequencies and/or increasing  $\beta_c$  of JJs.

# Energy and delay comparison

## Basic gate: Energy vs. delay

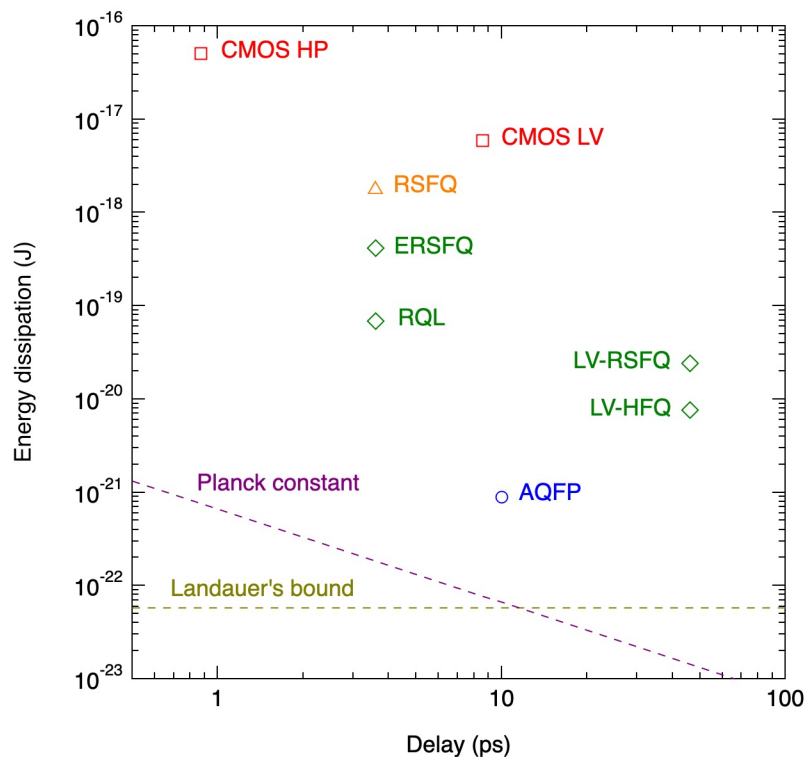

## Energy-delay product (EDP)


Logic	EDP (J·s)
CMOS HP	$4.4 \times 10^{-29}$
RSFQ	$6.3 \times 10^{-30}$
AQFP	$9.0 \times 10^{-33}$ (= 14h)

- CMOS: Inverter, AQFP: Buffer, others: JTL
- $I_c = 50 \mu\text{A}$  for all supercond. devices
- Delay of RSFQ, ERSFQ, RQL: 3.6 ps
- ERSFQ:  $2I_c\Phi_0 \times 2$  JJs [Mukhanov, IEEE TAS **21** (2011)]
- RQL:  $0.33I_c\Phi_0 \times 2$  JJs [Herr, JAP **109** (2011)]
- LV-HFQ, LV-RSFQ: Li, SuST **34** (2021)
- AQFP: Takeuchi, APL **115** (2019)

**AQFP operates with an extremely small EDP.**

# Minimal logic-gate design


**Building blocks (sub-cells)**

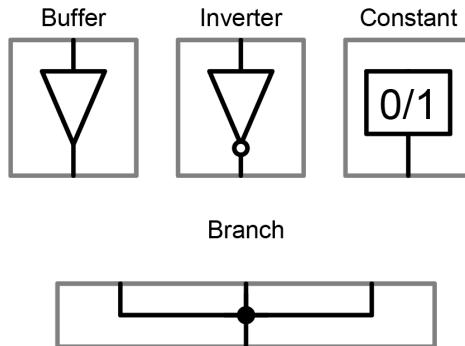

- Gate design based on majority logic:  $q = ab + bc + ca$
- Logic gates designed by placing four types of building blocks: buffer, inverter, constant, branch


N. Takeuchi et al., J. Appl. Phys. **117** (2015).

**Majority (MAJ)**

 


$$q = \text{MAJ}(a, b, c) \\ = ab + bc + ca$$

**AND**

 

$$q = \text{MAJ}(a, 0, c) \\ = ac$$


**NOR**

 

$$q = \text{MAJ}(\bar{a}, 0, \bar{c}) \\ = \bar{a}\bar{c} = \overline{(a+c)}$$

# Clocking schemes


## Four-phase clocking

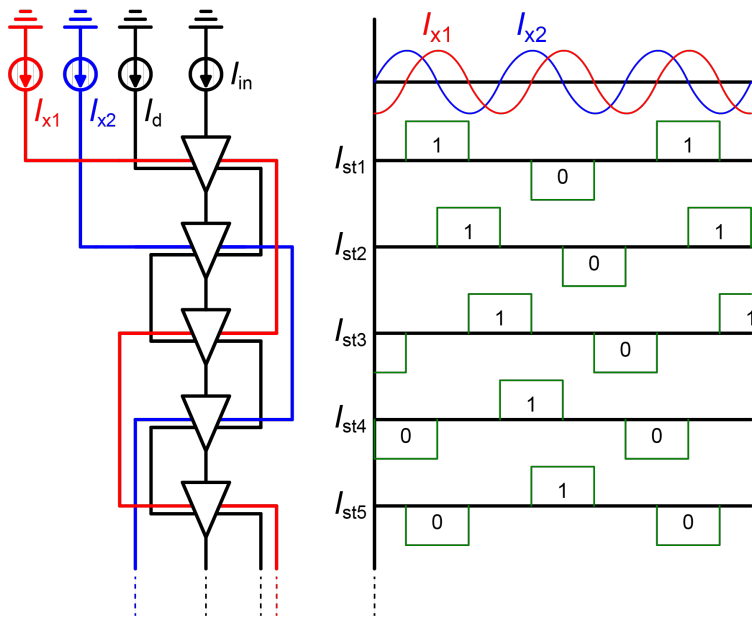

- × Latency: 1/4 clock cycle per gate
- ✓ Arbitrary clock frequency

W. Hioe et al., IEEE TAS **5** (1995).  
 N. Takeuchi et al., Supercond. Sci. Tech. **30** (2017).

## Delay-line clocking

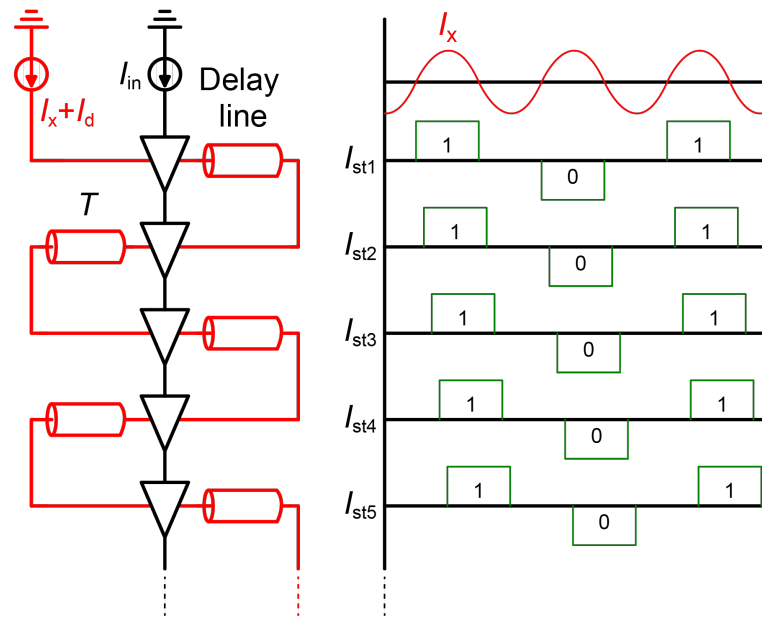


- ✓ Latency: arbitrary  $T$  per gate
- × Do not operate at low frequency

N. Takeuchi et al., Appl. Phys. Lett. **115** (2019).

# Circuit design example: Full adder


14

## Schematic diagram

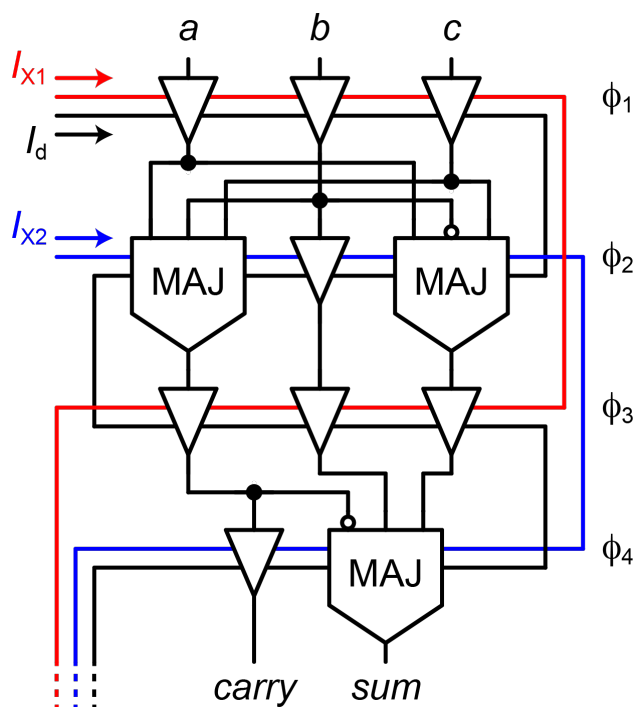

Additional buffers inserted for phase adjustment and multiple fanouts

## Layout

 


Excitation lines designed to be 50  $\Omega$  using InductEx

# Outline

15

- Introduction to AQFP logic
  - Adiabatic switching
  - Design methodology
- **Recent progress in AQFP logic**
  - Microprocessor
  - Single-photon image sensor
  - Stochastic electronics

# MANA microarchitecture

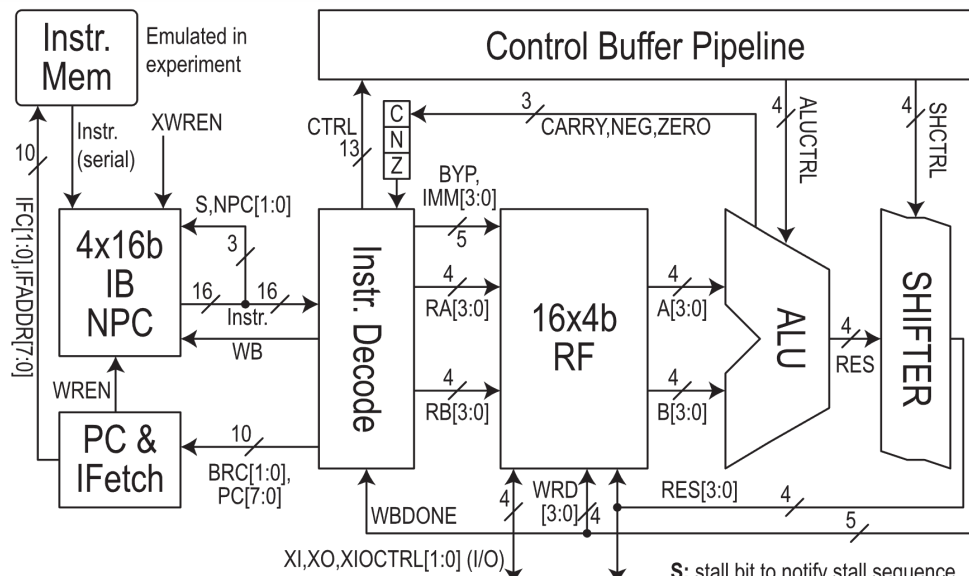

MANA instruction formats:

15	14	13	12	11	10	9	8	7	6	5	4	3	2	1	0						
S	NPC	OPCODE			IMM			RB			Immediate format										
S	NPC	OPCODE			BRC/JMP ADDR								Branch/jump format								
S	NPC	OPCODE			RA			RB								ALU format					
S	NPC	OPCODE			SOP		AMT		RB								Shifter format				
S	NPC	OPCODE			MEM											Memory access format					

**S:** stall bit to notify stall sequence  
**NPC:** next PC addr for IB  
**OPCODE:** opcode of instr.  
**IMM:** immediate value  
**BRC/JMP:** branch/jump addr.  
**RA:** reg. A addr.  
**RB:** reg. B addr. (also destination)  
**SOP,AMT:** shift opcode and amount  
**MEM:** Mem. addr. for data.

## MANA – Monolithic Adiabatic Integration Architecture

- **Goal:** Demonstrate AQFP can do both logic and memory
- RISC-like datapath + dataflow-like control
- In-order, single-issue
- 4-bit data word size
- 16-bit instr. word
- Program branching
- 21,460 JJs in 1 x 1 cm<sup>2</sup> chip
- 30 fJ/op at RT @ 5 GHz
- 4-phase 5 GHz clock
- Latency: 108 clock phases or 27 cycles (5.4 ns @ 5 GHz)

Instruction Buffer,  
 Decode, and Issue (IDI)  
 5,596 JJs  
 8 cycles (32 phases)

Register File  
 with external I/O (RFx)  
 8,142 JJs  
 8 cycles (32 phases)


ALU-Shifter  
 (EX)  
 2,238 JJs  
 9 cycles (36 phases)

Ctrl buffer, routing, write-back (WB)  
 5,484 JJs  
 17 cycles (68 phases) overlapped  
 2 cycles (8 phases) write-back




# MANA prototype chip

17

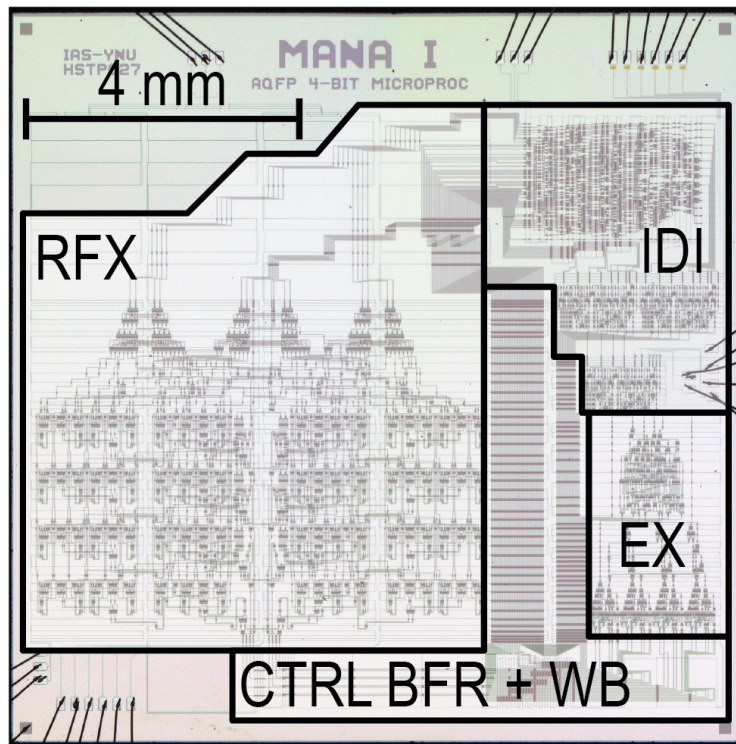


- MANA prototype chip
  - Nb/AIO<sub>x</sub>/Nb 10 kA/cm<sup>2</sup> technology
  - All stages integrated together by hand
  - 1 cm x 1 cm
  - Unoptimized clock network
  - Wire-bonded
  - 21,460 JJs
  - Latency: 27 cycles (5.4 ns @ 5 GHz)
- Experiment
  - Low-speed testing
  - 4x16-bit instruction blocks manually loaded to IB of IDI serially
  - 4-bit debug output tapped from WB data

# MANA high-speed test

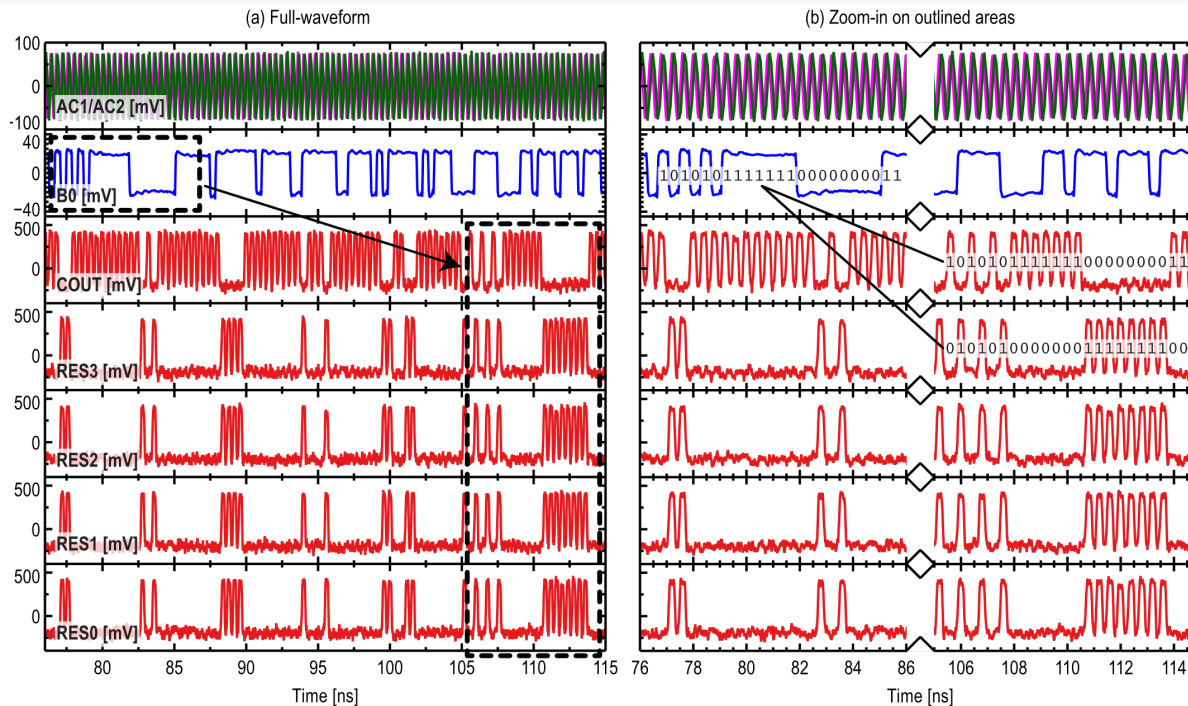

Critical carry-propagate  
 high-speed test pattern

(1111 + 0001)

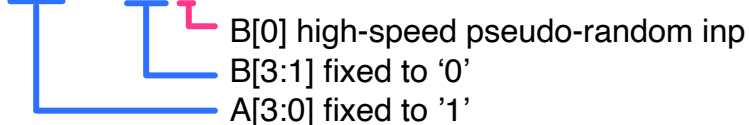


High-speed 2.5 GHz ( $T=400$  ps) test

- Expected outputs:  $COUT \leftarrow B[0]$ ;  $RES[3:0] \leftarrow !B[0]$
- 1 GHz ~ 2.5 GHz operated successfully
- 3 GHz operation unstable
  - ▣ Fall-time of output too slow, may need to improve output interface or experimental setup


# Reversible computing using AQFP

## Reversible QFP (RQFP)

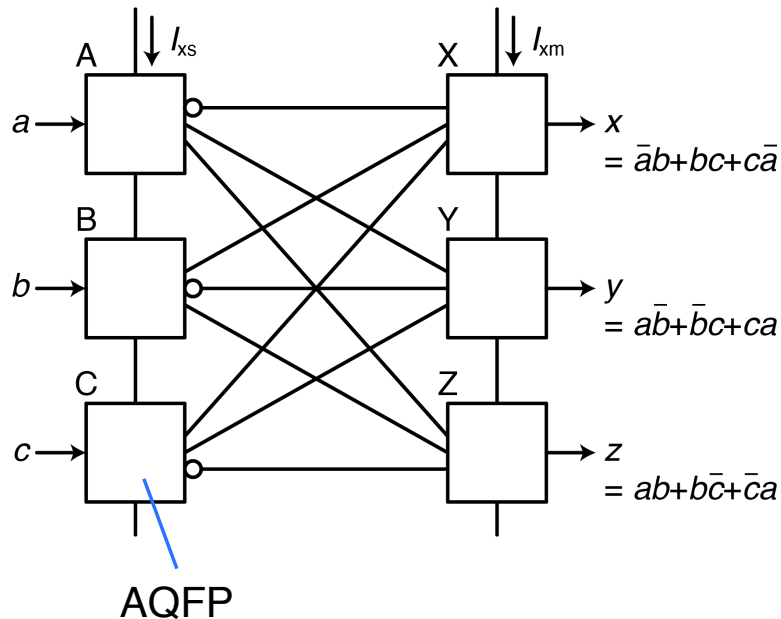

N. Takeuchi et al., Sci Rep. 7 (2017)
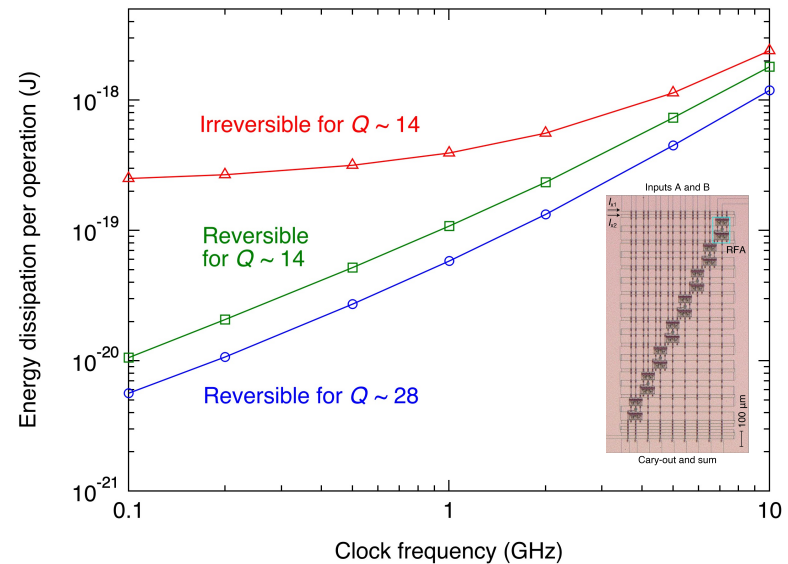
## Reversible vs. irreversible 8-bit adders



N. Takeuchi et al. ASC 2020.

- Reversible circuits can be designed using RQFP gates.
- Dissipation further decreases: -73% @ 1 GHz, -96% @ 100 MHz


# Outline

20

- Introduction to AQFP logic
  - Adiabatic switching
  - Design methodology
- **Recent progress in AQFP logic**
  - Microprocessor
  - Single-photon image sensor
  - Stochastic electronics


# Features for detector applications

## Low-current operation

 


- ✓ AC flux bias
- ✓ Many gates can couple to a few common bias lines.
- ✓ Total bias current (2–3 mA) does not increase w/ gate #.

## High sensitivity

 


- ✓ Adiabatic switching
- ✓ Can switch to the correct state w/ small input current
- ✓ Demonstrated a ~50 nA sensitivity

N. Takeuchi et al., IEEE TAS 31 (2021).

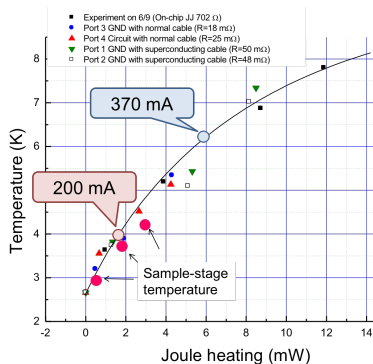

- Total supply current limited in a compact cryocooler
- Max. supply current: ~200 mA @ 0.1-W GM cooler

H. Terai et al., ASC2014.

 


- Sensitivity required for NbTiN SSPDs: ~10 μA
- WSi-SSPD: ~1 μA
- TES: less than 1 μA
- cf. Sensitivity of SFQ circ.: 1–10 μA

# Single-photon image sensor



22
 
## Superconducting nanowire single-photon detector (SSPD)




- ✓ High efficiency
- ✓ High count rate
- ✓ Low timing jitter
- ✓ Low dark count
- ✓ Wide spectral range

Original paper: G. N. Gol'tsman et al.,  
Appl. Phys. Lett. **79** (2001).

- Single pixel technology matured; multi-pixel array under development
- Efficient readout scheme required
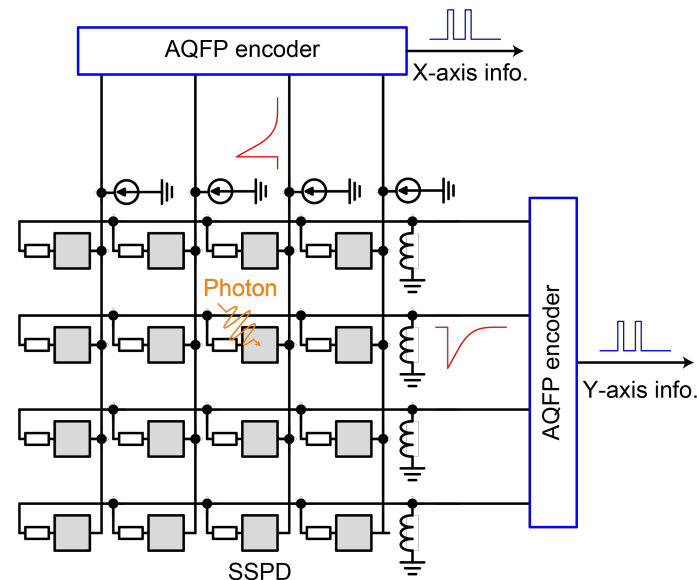
## Single-photon image sensor using SSPDs and AQFP




- ✓ AQFP used as an interface for SSPDs to reduce cable #
- ✓ Reduces heat inflow via cables


# SSPD array demonstrated using AQFP

23


## AQFP/RSFQ hybrid interface

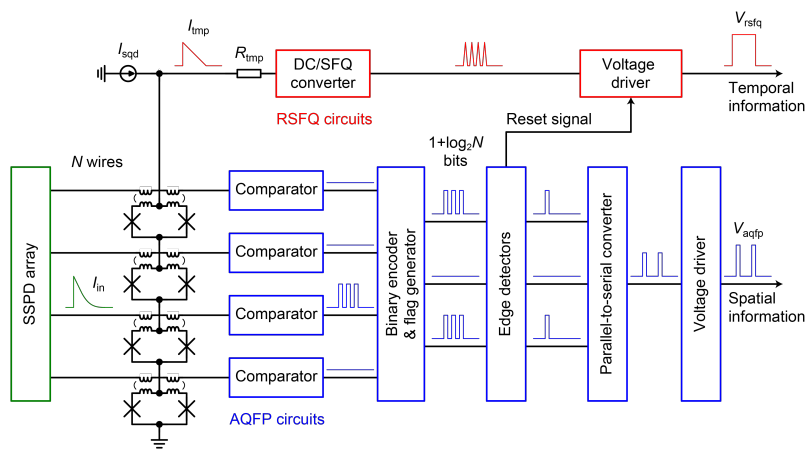

## Measurement waveform

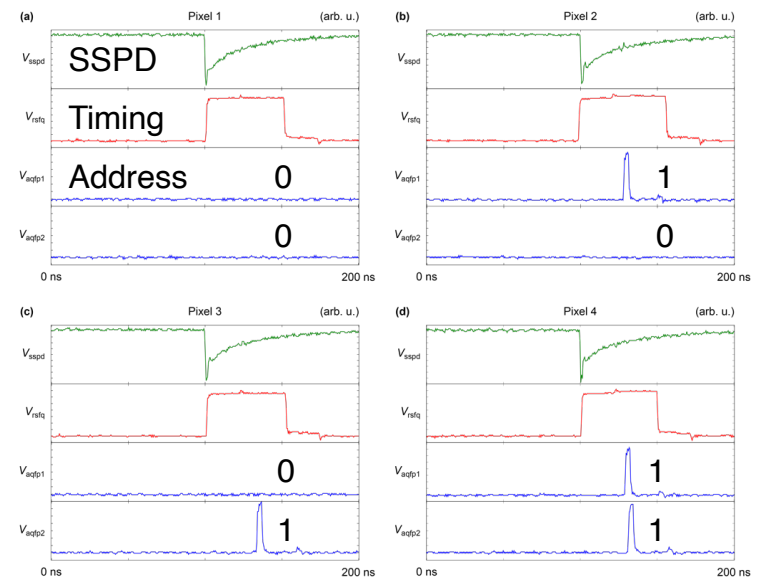

## Setup using a 0.1-W GM cooler

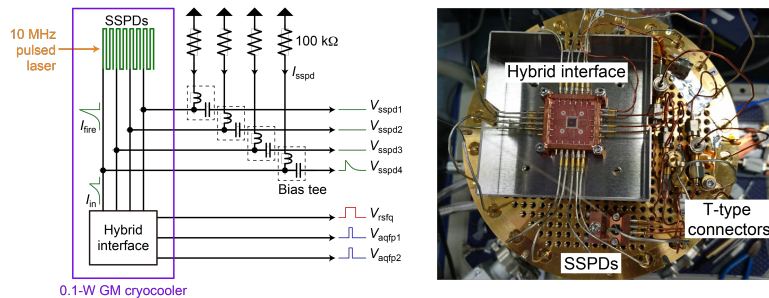

- Demonstrated a 4-px SSPD array using an AQFP/RSFQ interface
- All pixels read out with low error rates and low timing jitters

N. Takeuchi et al., Opt. Express **28** (2020).

# Outline

24

- Introduction to AQFP logic
  - Adiabatic switching
  - Design methodology
- **Recent progress in AQFP logic**
  - Microprocessor
  - Single-photon image sensor
  - Stochastic electronics




# Stochastic operation using thermal noise

25


For large input,

 - Logic state switches deterministically.
- Entropy change:  
 $\Delta S = 0$



For small input,

 - Logic state switches stochastically.
- Entropy change:  
 $\Delta S = \beta Q > 0$




- ✓ Can implement stochastic logic operation via thermal fluctuations
- ✓ Entropy change  $\Delta S$  can be controlled by input current amplitude.


# Random number generator

26

## AQFP buffer

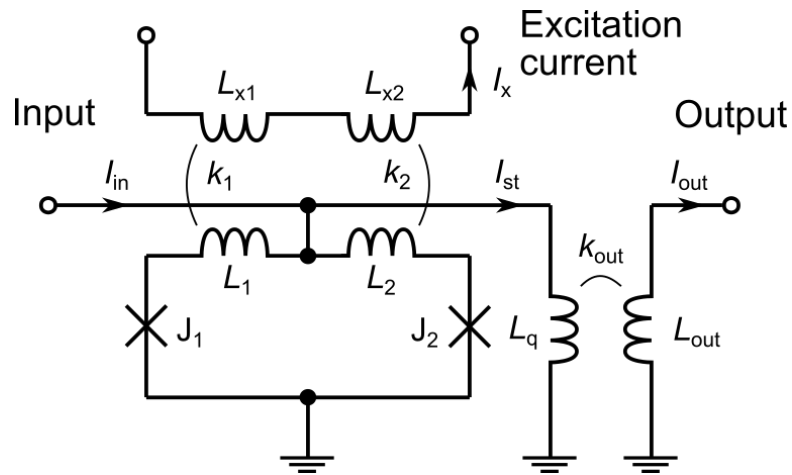

## Simulation


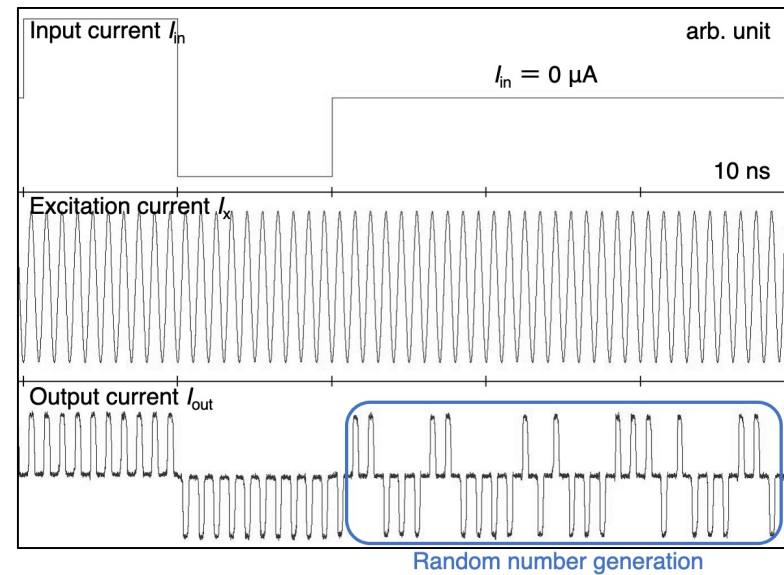


W. Luo et al., IEEE TAS 31 (2021).

An AQFP buffer can be used as a random number generator.

# Stochastic local search (SLS) solver

## AQFP-based SLS solver

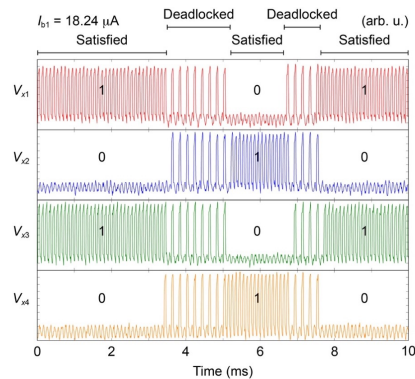
 


Find a vector  $\mathbf{x} = (x_1, x_2, x_3, x_4)$   
 such that  $x_i = \text{NOR}(x_{i-1}, x_{i+1})$ .

- Demonstrated SLS for a simple logical constraint sat. problem
- Solutions quickly found with moderate fluctuations

N. Takeuchi et al., Phys. Rev. Appl. **11** (2019).  
 M. Aono, Jpn. J. Appl. Phys. **59** (2020).

## Solution-search speed meas.

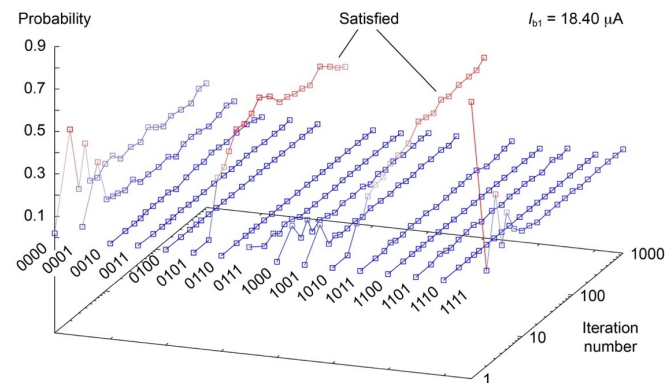 

# Summary

28

- **AQFP: energy-efficient logic device**
  - $\sim 10^{-21}$  J per gate at 5 GHz due to adiabatic switching
  - Majority logic, minimal design, ac flux biasing
  
- **Recent Progress in AQFP**
  - Microprocessor
    - 4-bit prototype demonstrated (ALU tested @ 2.5 GHz)
    - Reversible processor also being developed
  - Single-photon image sensor
    - 4-px system demonstrated
  - Stochastic electronics
    - Random number generator and SLS solver demonstrated
  
- For more details, see: N. Takeuchi et al., “Adiabatic Quantum-Flux-Parametron: A Tutorial Review,” IEICE Trans. Electron., in press.
- Some of the slides were modified or omitted.

# Acknowledgements

29

- **The present study was supported by JSPS KAKENHI (Grants No. JP18H01493, No. JP18H05245, and No. JP19H05614).**
- **The circuits were fabricated in the Clean Room for Analog-digital superconductiVITY (CRAVITY) at the National Institute of Advanced Industrial Science and Technology (AIST).**
- **The authors would like to thank C. J. Fourie for providing a 3D inductance extractor, InductEx. The authors would like to thank all the collaborators.**